
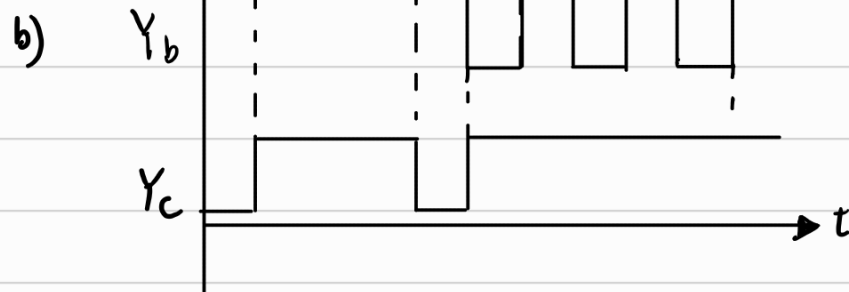
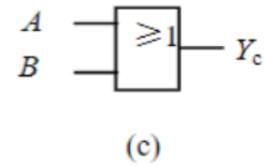
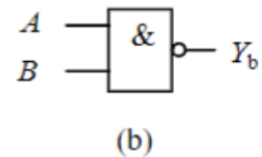


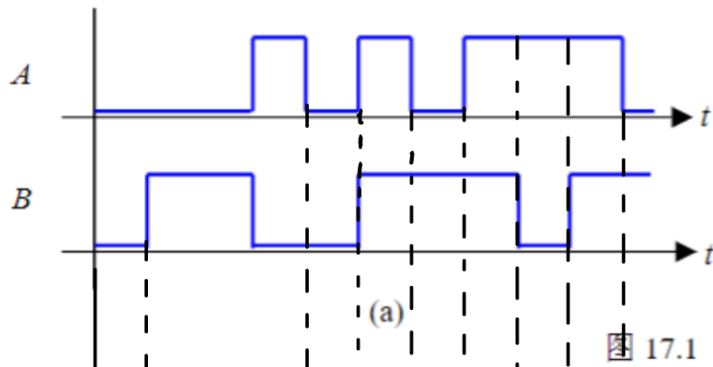17.1 (门电路功能) 作用于各门电路输入端的信号波形如图 17.1 (a) 所示。画出图 17.1 (b) (c) 各电路输出端 Y 的波形图。




17.2 (逻辑代数化简) Using Boolean algebra (布尔代数, 逻辑代数) techniques, simplify the following expression as much as possible, and implement the logic circuit using gate circuits.


(a) $X = (AB + \bar{A}\bar{B} + \bar{A}B)(A + B + D + \bar{A}\bar{B}\bar{D})$

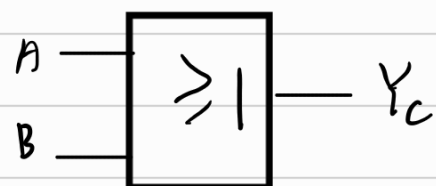(b) $X = \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D}$

$$\begin{aligned} a) X &= [A(B+\bar{B}) + \bar{A}\bar{B}](A+B+D+\bar{A}\bar{B}\bar{D}) \\ &= (A+\bar{A}\bar{B})(A+B+D+\bar{A}\bar{B}\bar{D}) \\ &= (A+\bar{B})(A+B+D+\bar{A}\bar{B}\bar{D}) \\ &= (A+\bar{B})(A+B+D+\bar{A}+\bar{B}+\bar{D}) \\ &= (A+\bar{B})(A+\bar{A}+B+\bar{B}+D+\bar{D}) \\ &= A+\bar{B} \end{aligned}$$


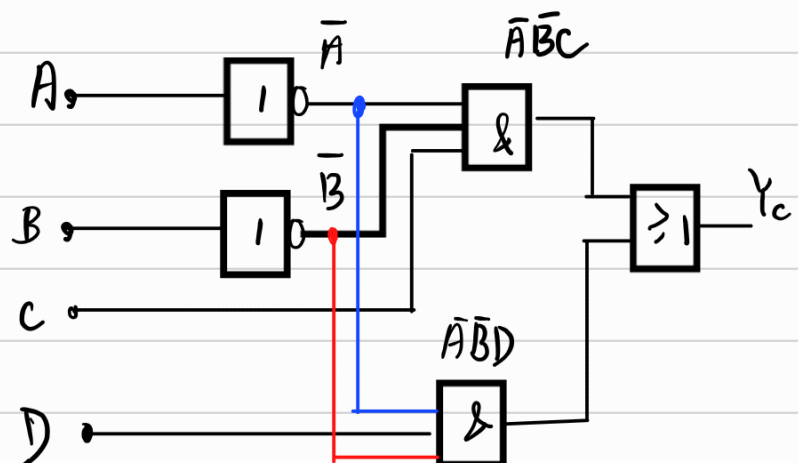
$$\begin{aligned} b) X &= \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} \\ &= \bar{A}\bar{B}(C+\bar{C}) + \bar{A}B\bar{C}(D+\bar{D}) \\ &= \bar{A}\bar{B}(C+\bar{C}) + \bar{A}B\bar{C}(D+\bar{D}) \\ &= \bar{A}\bar{B}C + \bar{A}B\bar{C} \end{aligned}$$



17.3 (卡诺图化简) Use a Karnaugh map to simplify the following expression to a minimum sum-of-product form (积和式, 与或式), and implement the logic circuit using NAND gates (与非门).

$$A\bar{B}(C+\bar{C}) \quad (D(A+\bar{A}))$$

(a) $Y = \bar{A}\bar{B} + \bar{A}\bar{B}\bar{C}D + CD + \bar{B}\bar{C}D + ABCD$

(b) $Y = AC + ABD + BC + BD$

a)

AB \ CD	00	01	11	10
00	0	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	1	1	1

Groupings: $\bar{B}$ (blue circle), $\bar{C}D$ (yellow oval), CD (red oval), BD (red oval).

$$A\bar{B}C + A\bar{B}\bar{C} + ACD + \bar{A}\bar{C}D$$


$$A\bar{B}C(D+\bar{D}) + A\bar{B}\bar{C}(D+\bar{D}) + ACD(B+\bar{B}) + \bar{A}\bar{C}D(B+\bar{B})$$

$$\bar{A}\bar{C}D(B+\bar{B})$$

$$= A\bar{B}CD + A\bar{B}\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + ABCD + \bar{A}\bar{B}CD + \bar{A}\bar{B}\bar{C}D$$

$$\bar{B}\bar{C}D(A+\bar{A}) = A\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}D$$
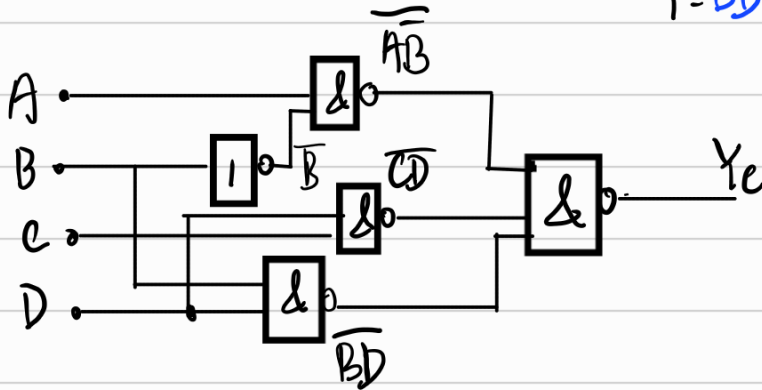
$$Y = \bar{B}D + \bar{C}D + \bar{A}\bar{B} = \overline{\bar{B}D \cdot \bar{A}\bar{B} \cdot \bar{C}D}$$




b)

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	0	1	1	1
10	0	0	1	1

Groupings: BC (blue circle), BD (green circle), AC (red circle).

$$Y = BC + AC + BD$$
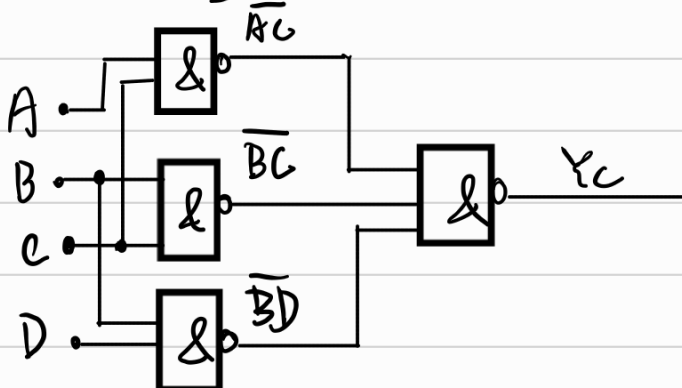
$$= \overline{\bar{B}\bar{C} \cdot \bar{A}\bar{C} \cdot \bar{B}\bar{D}}$$




17.4 (卡诺图化简) 利用卡诺图化简


(a) $F(A, B, C) = \Sigma(2, 3, 4, 6)$

(b) $F(A, B, C, D) = \Sigma(0, 1, 2, 3, 4, 6, 8, 9, 10, 11, 12, 14)$

a)

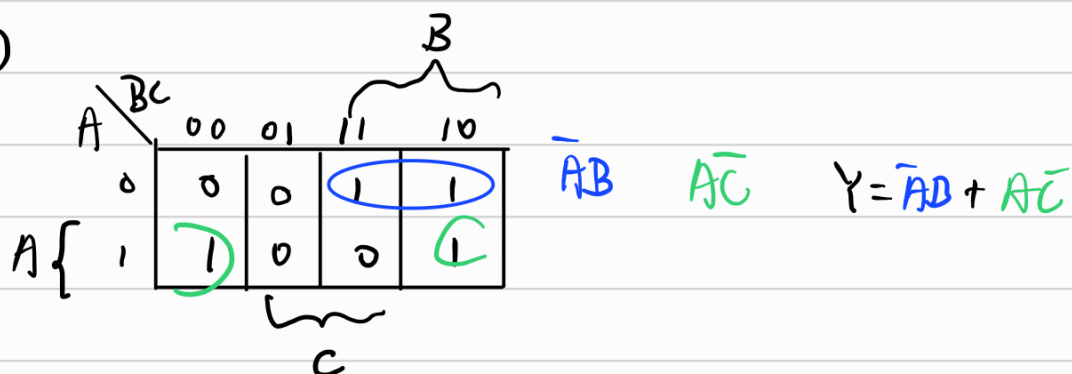


b)

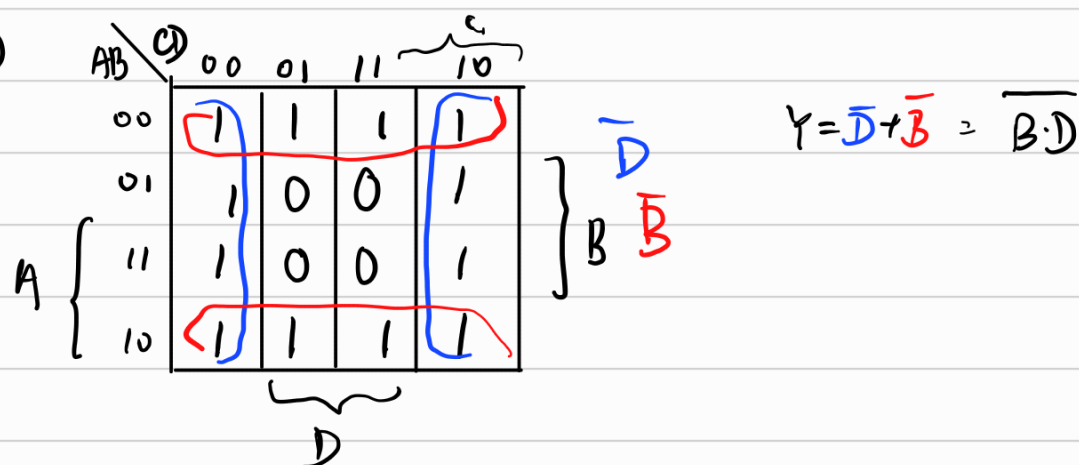

17.5 （卡诺图化简、逻辑代数化简综合题）已知逻辑函数 F 的真值表如图 17.5 所示（未给出的项为任意项），先用卡诺图化简法并再进一步用逻辑代数化简法写出 F 的最简表达式，使 F 可以用尽量少的门电路实现。

A	B	C	D	F
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	1	1
0	1	1	0	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0

图 17.5

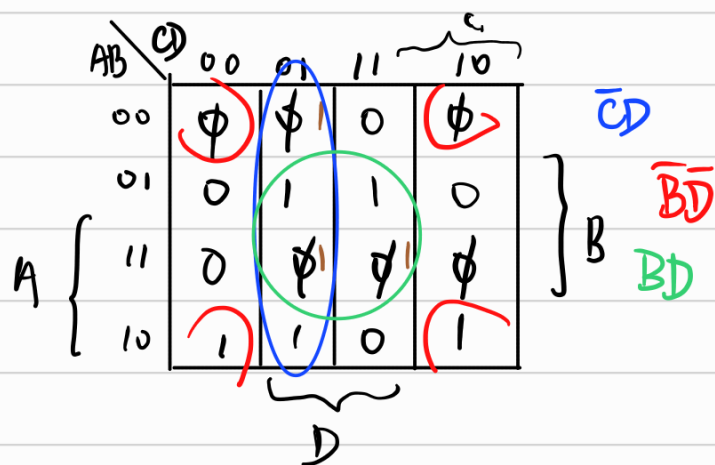

$$F = \bar{C}D + \bar{B}\bar{D} + B\bar{D}$$

