

实验 2-1:

$C = 1\mu\text{F}$										$R = \rule{1cm}{0.4pt}, L = \rule{1cm}{0.4pt}, f_0 = \rule{1cm}{0.4pt}, \Delta f = \rule{1cm}{0.4pt}$												
U/V	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	
f/Hz											f_0											
I/mA																						
$\varphi_{ui} \begin{cases} > 0 \\ = 0 \\ < 0 \end{cases}$																						
U_C/V																						
U_L/V																						
U_{C-L}/V																						
U_R/V																						

实验 2-2:

$C = 1\mu\text{F}$										$R = \rule{1cm}{0.4pt}, L = \rule{1cm}{0.4pt}, f_0 = \rule{1cm}{0.4pt}, \Delta f = \rule{1cm}{0.4pt}$											
U/V	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2	2
f/Hz											f_0										
I/mA																					
$\varphi_{ui} \begin{cases} > 0 \\ = 0 \\ < 0 \end{cases}$																					
U_C/V																					
U_L/V																					
U_{C-L}/V																					
U_R/V																					

实验 2-3:

$C/\mu\text{F}$	R/Ω	L/mH	f_0/Hz	$\Delta f/\text{Hz}$
U/V	I_0/mA	U_C/V	U_L/V	U_R/V