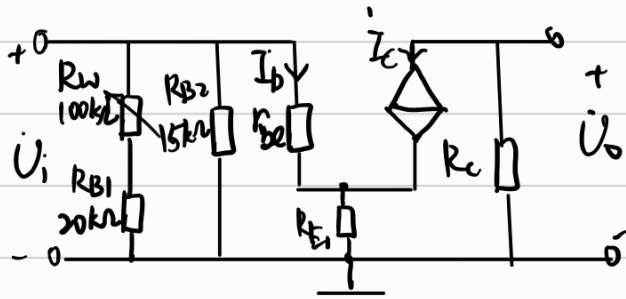


一、实验目的

- (1) 学习用 Multisim 实现电路仿真分析的主要步骤。
- (2) 用 Multisim 的仿真手段对电路性能作较深入的研究。

二、预习内容

(1) 计算静态工作点



$$U_E = 1.2V$$

$$\frac{R_{B2} V_{CC}}{R_W + R_{B1} + R_{B2}} = V_B = U_E + 0.7 = 1.9V$$

$$\frac{15k(12)}{R_W + 35k} = 1.9$$

$$R_W = 59.7368 k\Omega$$

$$I_E = \frac{U_E}{R_{E1} + R_{E2}} = \frac{1.2}{1200} = 1mA = I_C + I_B = (1+\beta)I_B \quad I_B = 16.3934 \mu A$$

$$I_C = \beta I_B = 983.6066 \mu A$$

$$r_{be} = 300 + (1+\beta) \frac{26}{I_E} = 1.886 k\Omega$$

$$U_{CE} = V_{CC} - I_C R_C - I_E (R_{E1} + R_{E2})$$

$$= 12 - 0.9836 \times 10^{-3} (3300) - 1 \times 10^{-3} (1200) = 7.5541 V$$

(2) 计算电压放大倍数 A_u

$$A_u = \frac{U_o}{U_i} = - \frac{\beta R_C}{r_{be} + (1+\beta) R_{E1}} = - \frac{60(3.3)}{1.886 + (61)(0.2)} = -14.0565 \approx -14.06$$

$$r_i = R_{B2} // (R_W + R_{B1}) // (r_{be} + (1+\beta) R_{E1}) = 6.6578 k\Omega$$

$$r_o = R_C = 3.3 k\Omega$$

将 R_{E1} 去掉并改变 R_{E2} 为 $1.2k\Omega$ ，静态工作点不变，则


$$A_u = -\frac{\beta R_c}{r_{be}} = -104.9841 \approx -104.98$$

$$r_i = R_{B2} // (R_w + R_{B1}) // r_{be} = 1.6409k\Omega$$


三、数据处理

实验 19-1

电路设计图如下：

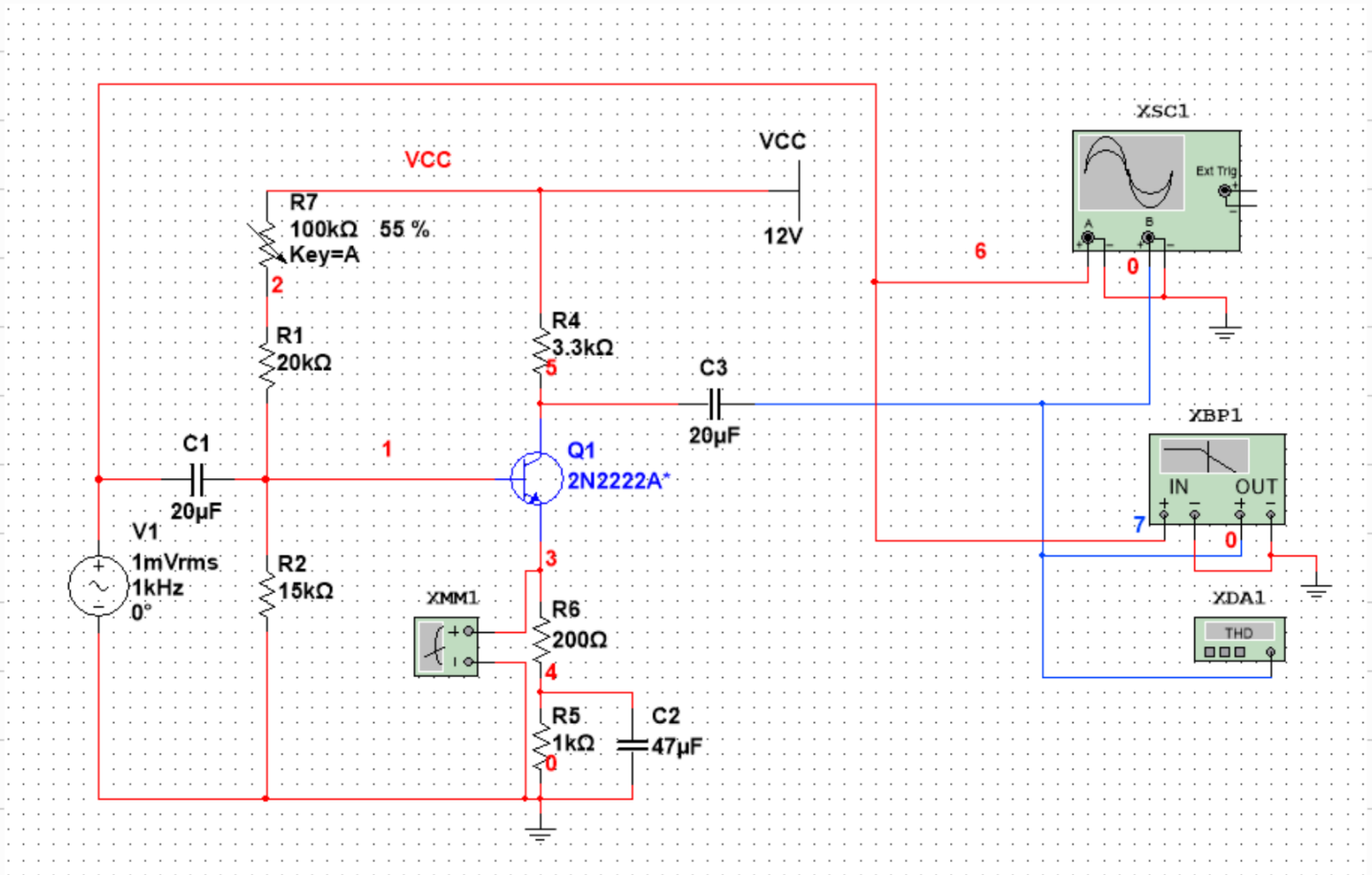


(1) 调节 R_w ，使 $V_E = 1.2V$

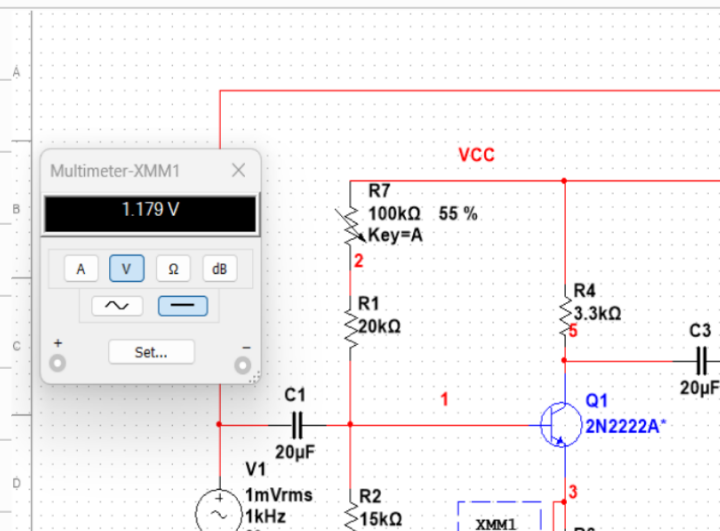

由上图可知,调节 R_W 至55%时,万用表测得 $U_E = 1.179V$ 。这符合计算得出的理论值
 $R_W(\text{理}) = 59.7368 k\Omega$ 。

(2) 测量静态工作点

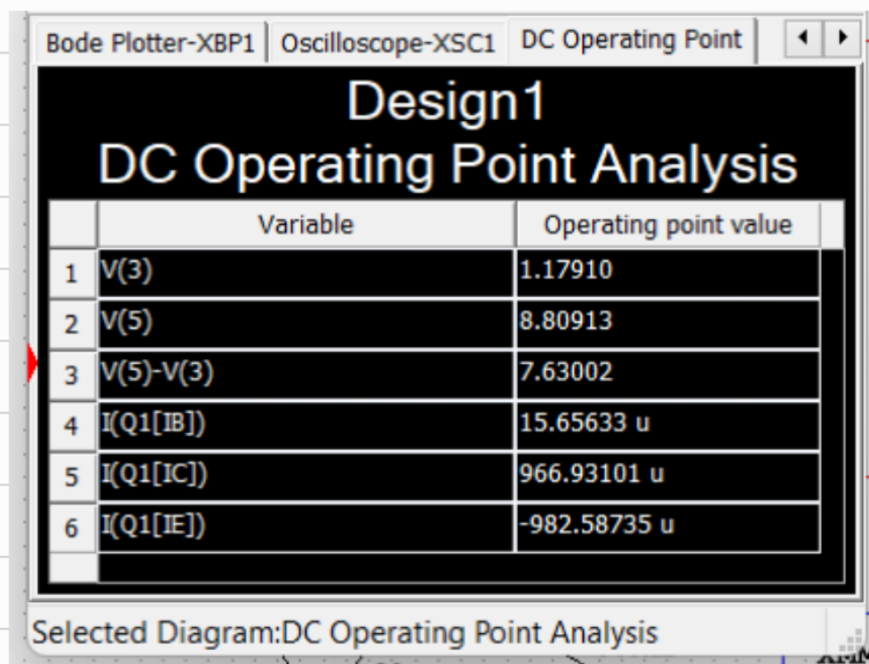

	Variable	Operating point value
1	V(3)	1.17910
2	V(5)	8.80913
3	V(5)-V(3)	7.63002
4	I(Q1[IB])	15.65633 u
5	I(Q1[IC])	966.93101 u
6	I(Q1[IE])	-982.58735 u

Selected Diagram: DC Operating Point Analysis

$$I_{BQ} = 15.6563 \mu A, I_{CQ} = 966.9310 \mu A, I_{EQ} = -982.5874 \mu A, U_{CEQ} = 7.63 V$$

绝对误差:

$$\Delta I_{BQ}: \frac{116.3934 - 15.6563}{16.3934} \times 100\% = 4.4963\% \approx 4.5\%$$


$$\Delta I_{CQ}: \frac{1966.9310 - 983.6066}{983.6066} \times 100\% = 1.6954\% \approx 1.7\%$$

$$\Delta I_{EQ}: \frac{1 - 982.5874 + 1000}{1000} \times 100\% = 1.7413\% \approx 1.7\%$$

$$\Delta U_{CEQ}: \frac{17.5541 - 7.631}{7.5541} \times 100\% = 1.0048\% \approx 1.0\%$$

以上所有仿真计算值与理论值相差不大,基本吻合。

(3) 输入、输出电压波形



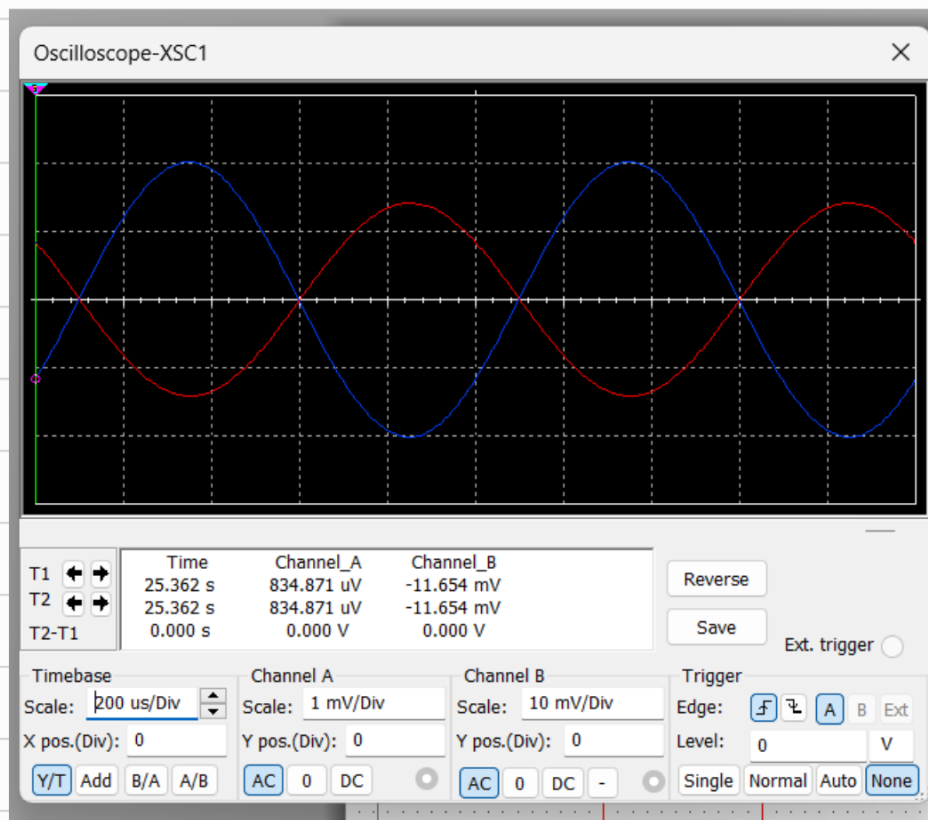


$$A_u = \frac{-11.654 \times 10^{-3}}{834.871 \times 10^{-6}} = -13.9590 \approx -13.96$$

$$\Delta A_u = \frac{1-13.96+14.06}{14.06} \times 100\% = 0.7112\% \approx 0.7\%$$

仿真计算值与理论值基本一致,吻合得较好。

(4) 波特图仪观察结果:

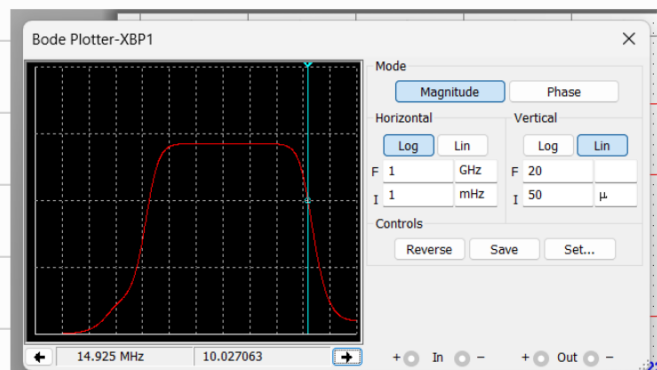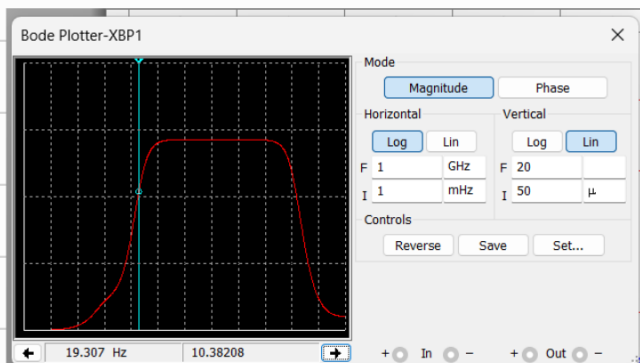
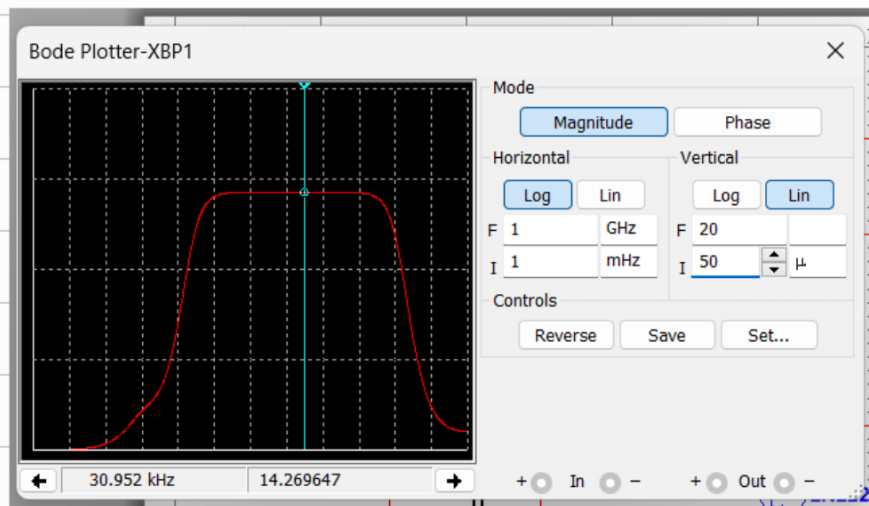


Y_{max} = 电压放大倍数 $A_u = 14.2696$, 截止频率: $f_c(Y_{max}) = 10.0901$

上限截止频率: 14.925 MHz 下限截止频率: 19.307 Hz

带宽 = $14.925 \text{ MHz} - 19.307 \text{ Hz} = 14924980.69 \text{ Hz} = 14.92498069 \text{ MHz}$

(5) 交流分析, 测量幅频特性和相频特性

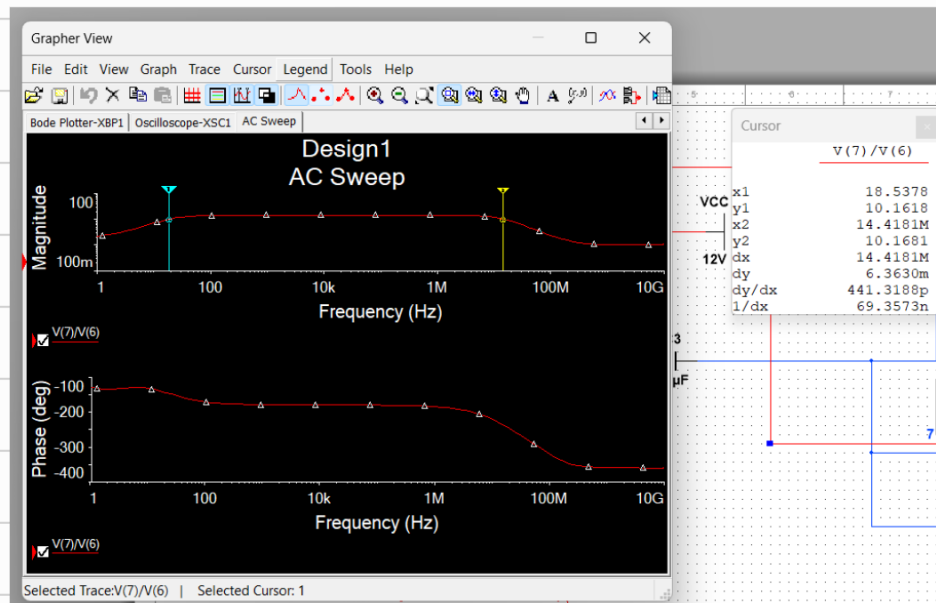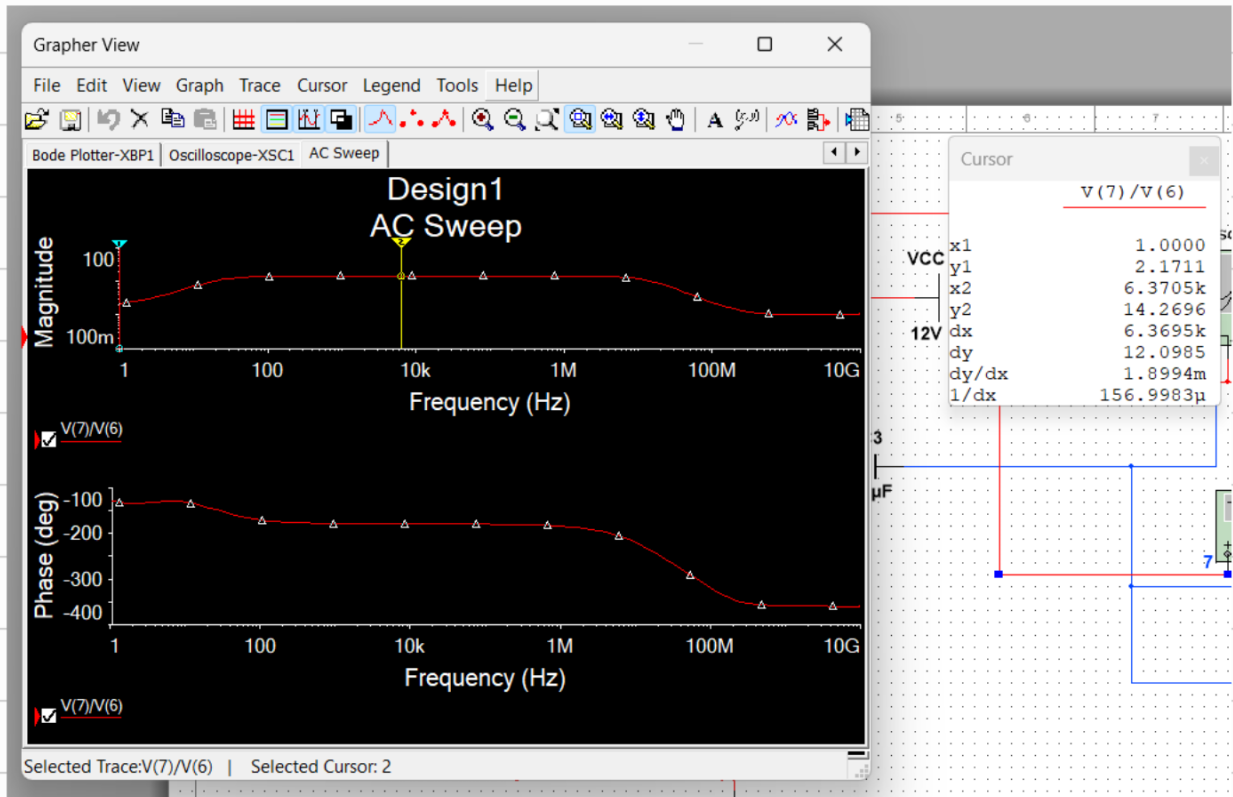

上限截止频率: 14.4181 MHz 下限截止频率: 18.5378 Hz


带宽 = $14.4181 \text{ MHz} - 18.5378 \text{ Hz} = 14418081.46 \text{ Hz} = 14.418081 \text{ MHz}$

与波特图仪结果相同。

从相位图也可看出频率越高, 相位差也越大。

(6) 加大输入信号幅度, 观测输出电压波形出现失真。

增大输入电压幅值, 增大到500mV时, 输出电压发生明显顶部失真。

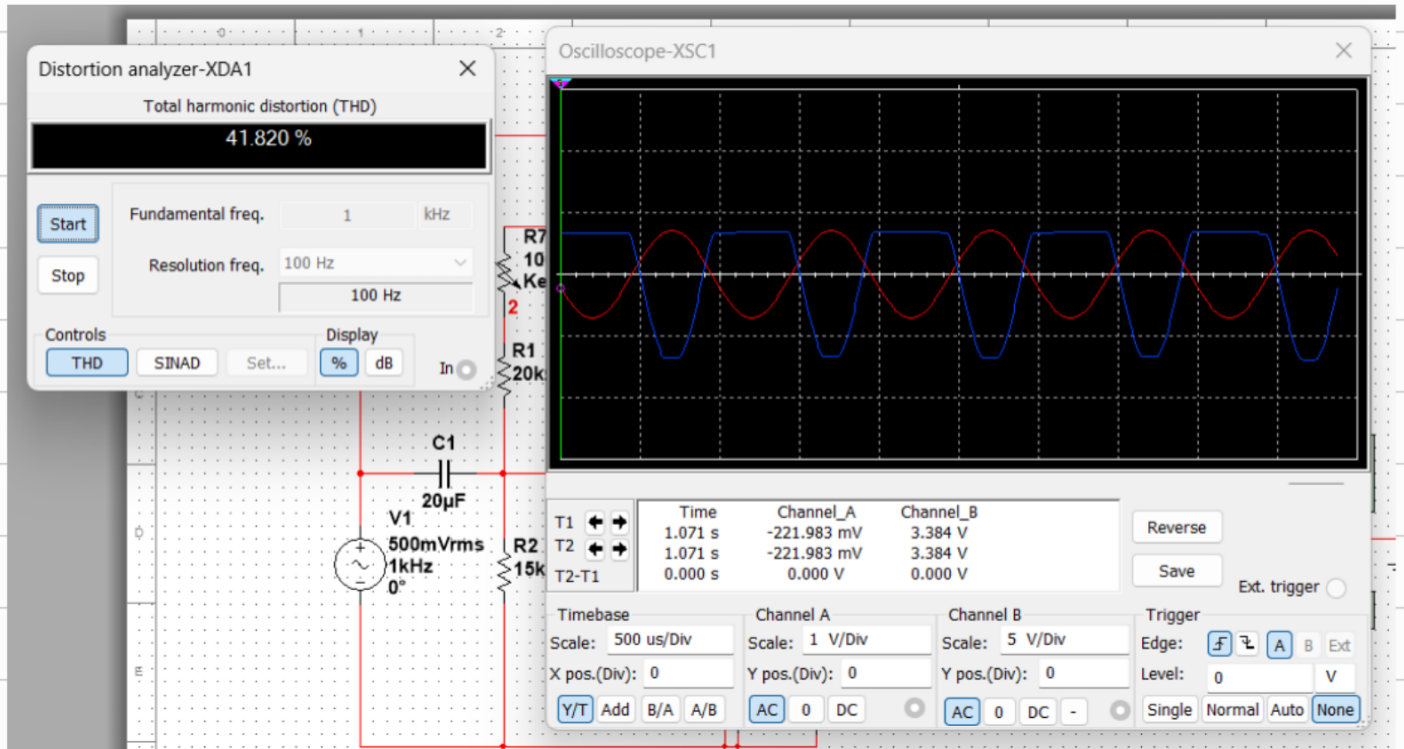


可通过失真度分析仪知道此时失真度为41.82%。

(7) 测量输入电阻 $r_i = U_i / I_i$; 输出电阻 $= (U_o / U_{o2} - 1) \times R_L$;


$$r_i = \frac{V(rms)}{I(rms)} = \frac{1 \times 10^{-3}}{152 \times 10^{-9}} = 6.5789 \text{ k}\Omega$$

$$\Delta r_i = \frac{16.6578 - 6.5789}{6.5789} \times 100\% = 1.1851\% \approx 1.2\%$$

与理论计算值基本吻合。

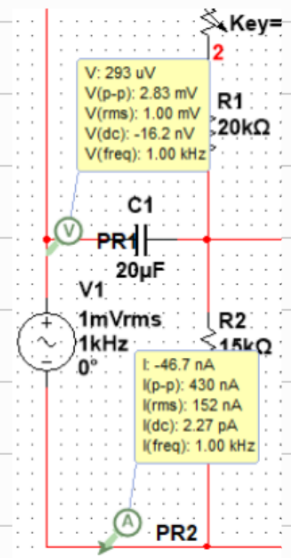


带载时 (接入 $R_L = 10k\Omega$), 输出电压的波形:

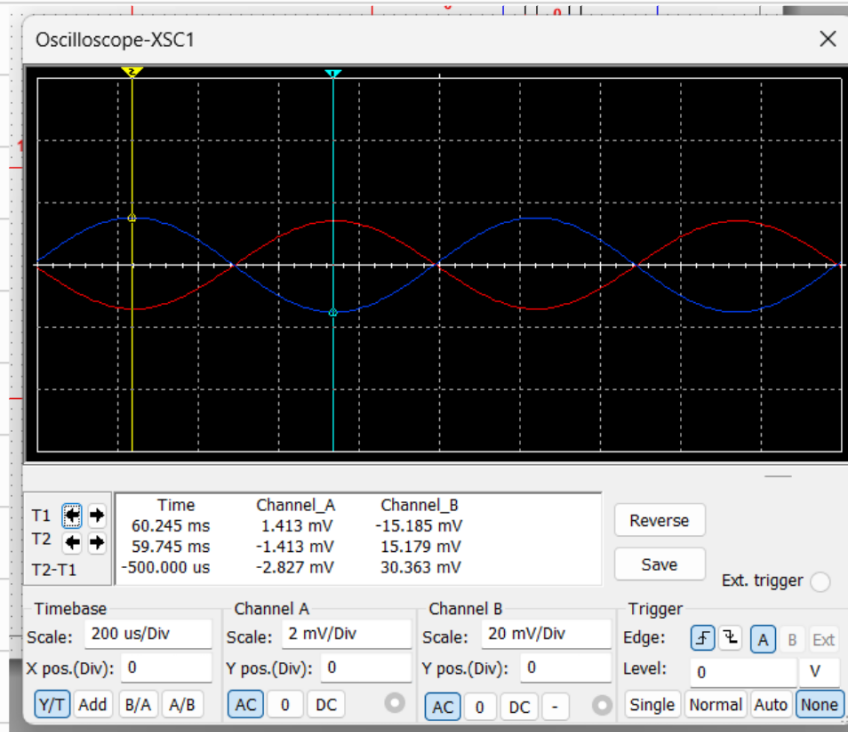

幅值 $U_{OL} = 15.182 \text{ mV}$

空载时, 输出电压波形:

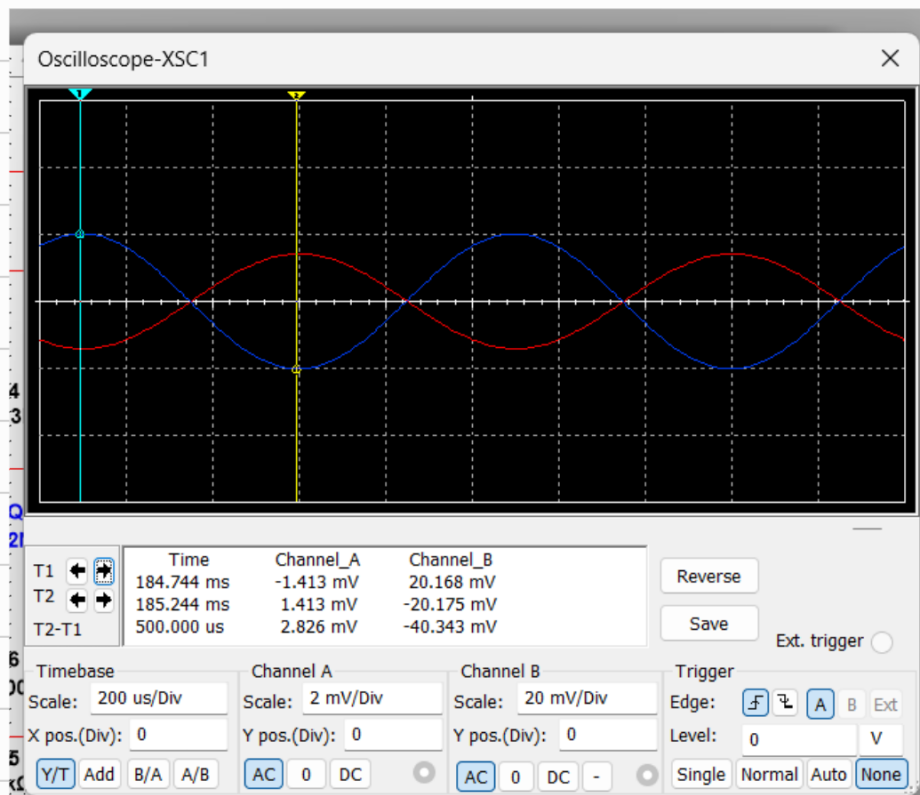


幅值 $U_o = 20.1715 \text{ mV}$

$$r_o = \left(\frac{U_o}{U_{OL}} - 1 \right) \times R_L = \left(\frac{20.1715}{15.182} - 1 \right) (10000) = 3.2868 \text{ k}\Omega$$




$$\Delta r_0 = \frac{13300 - 328651}{3300} \times 100\% = 0.9545\% \approx 1.0\%$$

可以认为仿真值与理论值一致。

18) 将 R_{E1} 去掉并改变 R_{E2} 为 $1.2k\Omega$

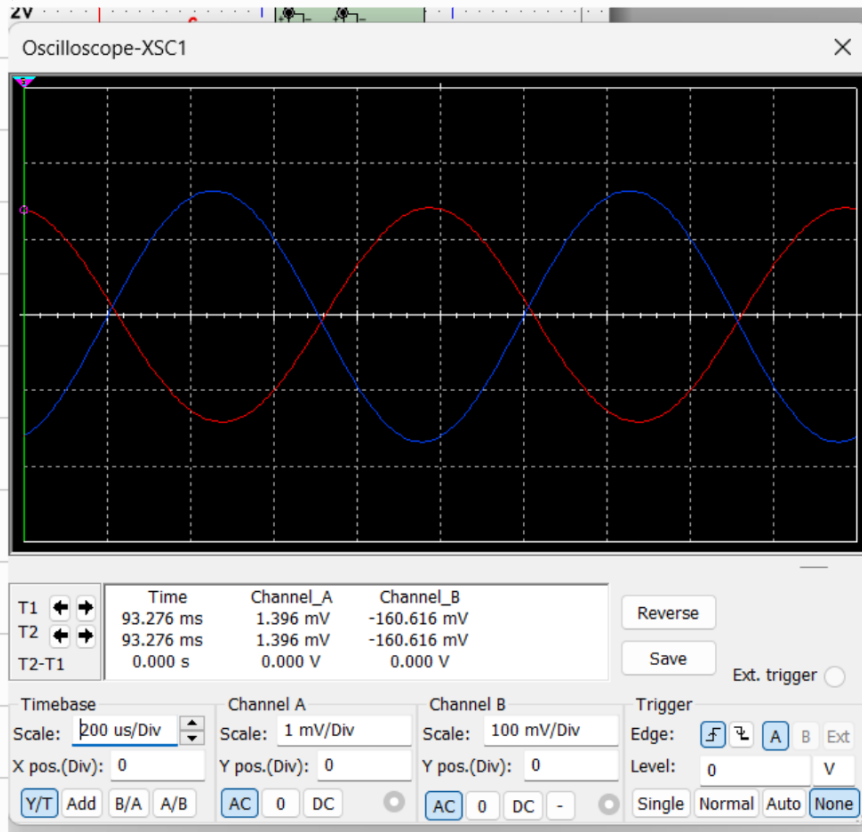
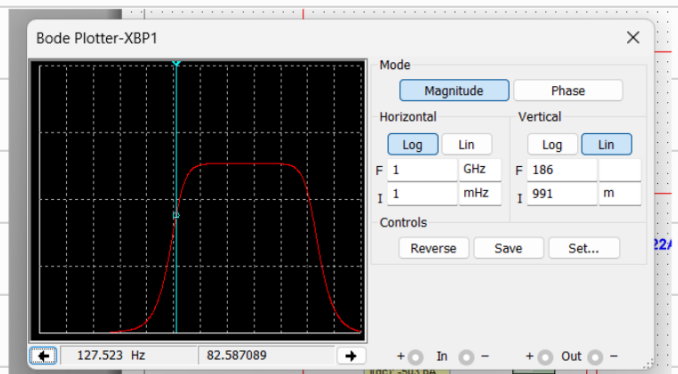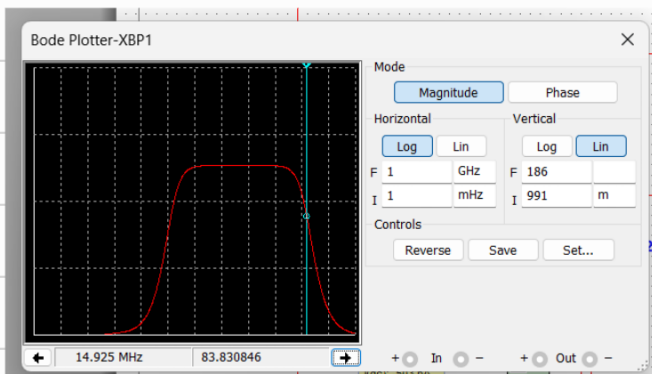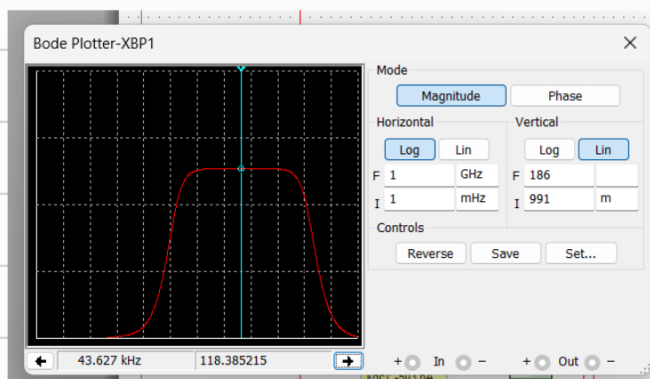
$$\text{电压放大倍数 } A_u = \frac{-160.616 \times 10^{-3}}{1.396 \times 10^{-3}} = -115.0544 \approx -115.05$$



$$Y_{max}' = \text{电压放大倍数} A_{u'} = -118.385215 \quad Y_{max}' * \frac{E_s}{E_i} = 83.711$$

上限截止频率: 14.925 MHz 下限截止频率: 82.587089 Hz

带宽: $14.925 \text{ MHz} - 82.587089 \text{ Hz} = 14924917.41 \text{ Hz}$

$\approx 14.92491741 \text{ MHz}$

$$\text{输入电压 } r_i = \frac{1 \times 10^{-3}}{6.7 \times 10^{-9}} = 1.4881 \text{ k}\Omega$$

列表前后对比:

	更改前	更改后
电压放大倍数	-13.96	-118.39
输入电阻	65789 $\text{k}\Omega$	1.4881 $\text{k}\Omega$
上下限截止频率	14.925 MHz, 19.307 Hz	14.925 MHz, 82.587 Hz

对比可知 R_{E1} 的存在使电压放大倍数减小, 输入电阻增大, 增大通频带宽。

